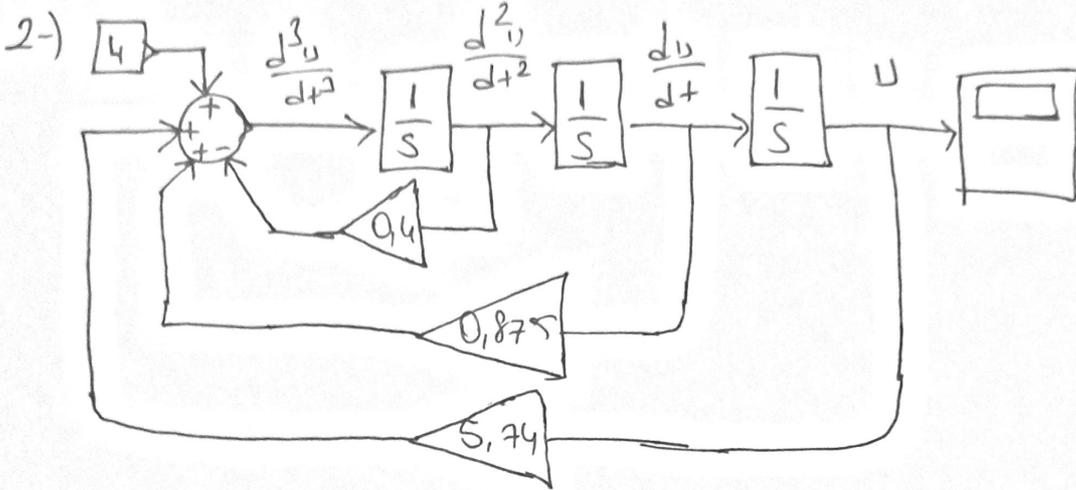


Q071/MLER

1- $u(2) * u(1)^2 + \text{sqrt}(u(2)) + u(1) * u(3)$




3- $V_t(t) = V_R(t) + V_L(t)$

$$V_t(t) = I(t) \cdot R + L \cdot \frac{dI(t)}{dt}$$

$$V_t(s) = I(s) \cdot R + L \cdot s \cdot I(s)$$

$$\frac{I(s)}{V_t(s)} = \frac{1}{2s + R} = \frac{1}{L} \left(\frac{1}{s + \frac{R}{L}} \right)$$
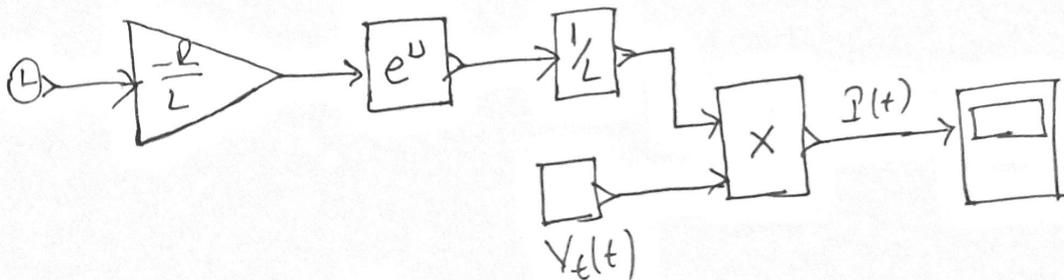
$$\frac{I(t)}{V_t(t)} = \frac{1}{L} \left(e^{-R \cdot t / L} \right)$$



→ Simulink Model.